

VHDL Code for SR Flip Flop:-


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity sr_flip_flop is
    port(
        s : in STD_LOGIC;
        r : in STD_LOGIC;
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        q : out STD_LOGIC;
        qb : out STD_LOGIC
    );
end sr_flip_flop;

architecture sr_flip_flop_arc of sr_flip_flop is
begin

    srff : process (s,r,clk,reset) is
    begin
        if (reset='1') then
            q <= '0';
            qb <= '1';
        elsif (rising_edge (clk)) then
            if (s/=r) then
                q <= s;
                qb <= r;
            elsif (s='1' and r='1') then
                q <= 'Z';
                qb <= 'Z';
            end if;
        end if;
    end process srff;

end sr_flip_flop_arc;
```

 

VHDL Code for D Flip Flop:-

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity tff_using_dff is
    port(
        clk : in STD_LOGIC;
        t : in STD_LOGIC;
        reset : in STD_LOGIC;
        dout : out STD_LOGIC
    );
end tff_using_dff;

architecture tff_using_dff_arc of tff_using_dff is

    component d_flip_flop is
        port(
            clk : in STD_LOGIC;
            din : in STD_LOGIC;
            reset : in STD_LOGIC;
            dout : out STD_LOGIC
        );
    end component d_flip_flop;


    signal ip : std_logic;
    signal op : std_logic;

begin

    ip <= op xor t ;
    u0 : d_flip_flop port map (clk => clk,
                               din => ip,
                               reset => reset,
                               dout => op);

    dout <= op;

end tff_using_dff_arc;
```

 

VHDL Code for JK Flip Flop:-


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity jk_flip_flop is
    port(
        j : in STD_LOGIC;
        k : in STD_LOGIC;
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        q : out STD_LOGIC;
        qb : out STD_LOGIC
    );
end jk_flip_flop;

architecture jk_flip_flop_arc of jk_flip_flop is
begin

    jkff : process (j,k,clk,reset) is
        variable m : std_logic := '0';
    begin
        if (reset='1') then
            m := '0';
        elsif (rising_edge (clk)) then
            if (j/=k) then
                m := j;
            elsif (j='1' and k='1') then
                m := not m;
            end if;
        end if;
        q <= m;
        qb <= not m;
    end process jkff;

end jk_flip_flop_arc;
```

 

VHDL Code for T Flip Flop:-

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity Toggle_flip_flop is
    port(
        t : in STD_LOGIC;
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        dout : out STD_LOGIC
    );
end Toggle_flip_flop;

architecture toggle_flip_flop_arc of Toggle_flip_flop is
begin

    tff : process (t,clk,reset) is
        variable m : std_logic := '0';
    begin
        if (reset='1') then
            m := '0';
        elsif (rising_edge (clk)) then
            if (t='1') then
                m := not m;
            end if;
        end if;
        dout <= m;
    end process tff;

end toggle_flip_flop_arc
```

