

**Experiment -1:** Write a VHDL code for all the logic gates

Objective:

The objective of this experiment is to:

- i. To revise the working of various logic gates
- ii. To learn the VHDL coding
- iii. To simulate for functional verification
- iv. To implement on CPLD / FPGA

**1. TITLE: AND gate**

**TRUTH TABLE:**

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

**Logic Equation:**

$$Z = X.Y$$

**This equation can be used for describing the dataflow model of AND architecture**

**We observe that the output is high when both X and Y are high '1', otherwise the output is low '0'. The property can be used in modeling the sequential behaviour**

**VHDL CODE:**

```
Library IEEE;
use IEEE.std_logic_1164.all;
entity AND2 is
    port(
        A : in STD_LOGIC;
        B : in STD_LOGIC;
        C : out STD_LOGIC
```

```
);  
end AND2;
```

-- The three architectural models are given below:


--1. *Dataflow model*

```
architecture behav1 of AND2 is  
begin  
    C <= A and B;    --Signal Assignment Statement  
end behav1;
```

-- 2. *Behavioral model*

```
architecture behav2 of AND2 is  
begin  
    process (A, B)  
    begin  
        if (A='1' and B='1') then  
            C<= '1';  
        else  
            C<= '0';  
        end if;  
    end process; end behav2;
```

**OUT PUT WAVE FORM:**

 

## 2. TITLE: OR gate

### TRUTH TABLE:

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

### Logic Equation:

- i.  $Z = X + Y$  This can be used for describing the dataflow model of AND architecture
- ii. We observe that the output is high when any or all the inputs X and Y are high '1', otherwise the output is low '0'. The property can be used in modeling the sequential behaviour

### VHDL CODE


```
Library IEEE;
use IEEE.std_logic_1164.all;
entity OR2 is
    port(
        x : in STD_LOGIC;
        y : in STD_LOGIC;
        z : out STD_LOGIC
    );
end OR2;
--Dataflow model
architecture behav1 of OR2 is
begin
    Z <= x or y;      --Signal Assignment Statement
end behav1;
-- Behavioral model
architecture behav2 of OR2 is
```

```

begin
  process (x, y)
  begin
    if (x='0' and y='0') then
      Z <= '0';
    else
      Z <= '1';
    end if;
  end process; end behav2;

```

### OUTPUT WAVEFORM:

 

### 3. TITLE: NOT gate

#### TRUTH TABLE:

x	z
0	1
1	0

1.  $Y = X'$  This can be used for describing the dataflow model of AND architecture
2. We observe that the output is high when inputs X low '0', and the output is low when input X is high '1'. The property can be used in modeling the sequential behavior

#### VHDL CODE:

```
Library IEEE;
use IEEE.std_logic_1164.all;
entity not1 is
    port(
        X:  in  STD_LOGIC;
        Y:  out STD_LOGIC
    );
end not1;

--Dataflow model
architecture behav1 of not1 is
begin
    Y<= not X; --Signal Assignment Statement
end behav1;


-- Behavioral model
architecture behav2 of not1 is
begin
    process (X)
```

```

begin
    if (x='0') then -- Compare with truth table
        Y<= '1';
    else
        Y<= '0';
    end if;
end process;
end behav2;

```

#### OUTPUT WAVEFORM for NOT Gate:

 

#### 4. TITLE: NAND gate

##### TRUTH TABLE:

x	y	z
0	0	1
0	1	1
1	0	1
1	1	0

- i.  $Y = (X.Y)'$  This can be used for describing the dataflow model of AND architecture
- ii. We observe that the output is high when any or all inputs X and Y are low '0', and the output is low when all input are high '1'. The property can be used in modeling the sequential behavior

##### VHDL CODE:

```

Library IEEE;
use IEEE.std_logic_1164.all;


entity nand2 is
    port(
        x : in STD_LOGIC;
        y : in STD_LOGIC;
        z : out STD_LOGIC
    );
end nand2;

--Dataflow model
architecture behav1 of nand2 is
begin
    z <= x nand y;           --Signal Assignment Statement
end behav1;

-- Behavioral model
architecture behav2 of nand2 is
begin
    Process (x, y)
    Begin
        If (x='1' and y='1') then
            Z <= '0';
        else
            Z <= '1';
        end if;
    end process; end behav2;

```

## OUTPUT WAVEFORM

 

## 5. TITLE: NOR gate

### TRUTH TABLE:

x	y	z
0	0	1
0	1	0
1	0	0
1	1	0

- i.  $Y = (X + Y)'$  This can be used for describing the dataflow model of AND architecture
- ii. We observe that the output is high when all inputs X and Y are low '0', and the output is low when any or all input are high '1'. The property can be used in modeling the sequential behavior

### VHDL CODE:

```
Library IEEE;
use IEEE.std_logic_1164.all;
entity nor2 is
    Port (
        X: in STD_LOGIC;
        Y: in STD_LOGIC;
        Z: out STD_LOGIC
    );
end nor2;
--Dataflow model
architecture behav1 of nor2 is
begin
    Z<= x nor y;
end behav1;
-- Behavioral model
architecture behav2 of nor2 is begin
```




```

process (x, y)
begin
--Signal Assignment Statement
    If (x='0' and y='0') then
        Z <= '1';
    else
        Z <= '0';
    end if;
end process;
end behav2;

```

#### OUTPUT WAVEFORM:

 

#### 6. TITLE:EX-OR gate

##### TRUTH TABLE:

- $Y = (X \cdot Y + X \cdot Y)$  This can be used for describing the dataflow model of AND architecture
- We observe that the output is low when all inputs X and Y are low '0' or when all the inputs are high. The output is high when any input is high '1'. The property can be used in modeling the sequential behavior

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0

## VHDL CODE:

Library IEEE;

use IEEE.std\_logic\_1164.all;

entity xor2 is

Port ( X: in STD\_LOGIC;

Y: in STD\_LOGIC;

Z: out STD\_LOGIC

);

end xor2;

*--Dataflow model*

architecture dataflow of xor2 is

begin

Z <= x xor y; *--Signal Assignment Statement*

end dataflow;

*--behaviour modelling*

architecture behav2 of xor2 is

begin

process (x, y)

begin

If (x/=y) then

Z <= '1';

else

Z <= '0';

end if;

end process;

end behav2;

## OUTPUT WAVEFORM

